



set n = 10
set R = 10000

$$\frac{\frac{R}{n-1}}{R + \frac{R}{n-1}} = \frac{10000}{10000 + \frac{10000}{10-1}} = 0.1 \text{ voltage attenuation}$$

note that value of R (if all the same) does not effect voltage attenuation - it does define buss impedance and buss impedance against the source impedances into the drop on resistors will effect crosstalk and noise performance

$$20 \left(\log \frac{\frac{10000}{10-1}}{10000 + \frac{10000}{10-1}} \right) 0.775 = -15.5 \text{ dBu buss level}$$

$$\frac{R}{n} = \frac{10000}{10} = 1000 \text{ ohm buss impedance}$$

- 1) pick a buss impedance - I'll pick 600 ohms
 - 2) how many drop on points (28)
 - 3) value of R will be 600 times 28 or 16.8K
 - 4) do the math
- $$20 \left(\log \frac{\frac{16800}{28-1}}{16800 + \frac{16800}{28-1}} \right) 0.775 = -22.5 \text{ dBu buss level}$$
- 5) set make up gain amp input impedance at 600 ohms
 - 6) buss level will drop 6dBu to -28.5 dBu
 - 7) you want to get up to +4dBu so total gain needed = +34.5 dB

